


1. Find force acting on a point charge  $q$  on  $z$  axis due to a ring of charge of radius  $a$  carrying uniform line charge density  $\rho_l$

- A.  $a * z / (2 \pi (z^2 + a^2)^{3/2}) a_z$
- B.  $a * z / (2 \pi (z^2 + a^2)^{3/2}) a_y$
- C.  $1 / (2 \pi (z^2 + a^2)^{3/2}) a_z$
- D.  $1 / (2 \pi (z^2 + a^2)^{3/2}) a_y$

2. One of the following complex power loads has a lagging power factor:

- A.  $S_L = 10 \text{ MW} + j 5 \text{ Mvar}$ .
- B.  $S_L = 10 \text{ MW} - j 5 \text{ Mvar}$
- C.  $S_L = 0 \text{ MW} - j 5 \text{ Mvar}$
- D.  $S_L = 10 \text{ MW} + j 0 \text{ Mvar}$

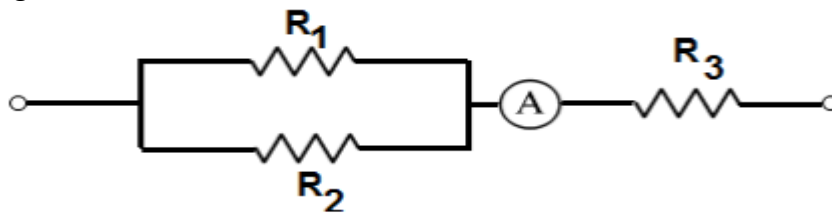3. Two resistors  $R_1 = 6 \Omega$  and  $R_2 = 12 \Omega$  are connected in parallel to each other and in series to  $R_3 = 2 \Omega$ . An ammeter measures an electric current of 3 A flowing through resistor  $R_3$ . What is the current in  $12 \Omega$  resistor?



- A. 6 A
- B. 1 A
- C. 3 A
- D. 5 A