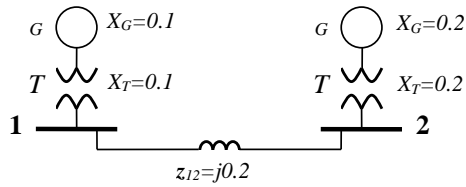


1. The system shown in the figure is running at no-load before a 3-phase fault occurs. All values are given in p.u. If a fault with fault impedance $j0.8$ p.u. occurs at bus 2, then, the fault current at bus 2, in p.u., is:



- A. $-j1.25$ p.u.
B. $-j2.50$ p.u.
C. $j1.00$ p.u.
D. **$-j1.00$ p.u.**
2. The resistance of an electric arc can be increased by
- A. Increasing the concentration of ionised particles.
B. Reducing the arc length.
C. **Splitting the arc.**
D. Increasing the arc cross section.

3. The value of Solar Constant is

- A. 1347 W/m^2
B. 1357 W/m^2
C. **1367 W/m^2**
D. 1377 W/m^2

